

DESKTOP AUDIO SYSTEM

Andrew Lynch

Kamal Sanghi

Chris Grahn

THE PROBLEM

- ▶ At any given time, there are multiple audio sources on my desk
 - ▶ MP3 player (iPod)
 - ▶ Desktop Computer
 - ▶ Laptop Computer
 - ▶ Police Scanner
- ▶ Most speaker systems allow one or possibly two inputs
- ▶ Lots of analog cables

THE PROBLEM

▶ Current Solution:

▶ Behringer DJ mixer

- ▶ Advantages: Allows mixing of up to four inputs, has line out to be passed to powered speakers
- ▶ Disadvantage: Large footprint on desktop, headphone level is product of main output level, all analog.

▶ Powered Logitech speakers


- ▶ Simple 2.1 sound system
- ▶ Audio quality is OK, but I'd like to use some nice bookshelf speakers instead

▶ All Analog


- ▶ Would rather use USB audio out of the computer, frees up the audio card on the desktop for other duties


▶ Proposed project: Combine these discrete components

REQUIREMENTS

- ▶ Mix up to four analog stereo inputs into one stereo output
 - ▶ Provide two USB->Audio converters built in
 - ▶ Hook up a computer via USB for audio, instead of analog
 - ▶ These will take the place of two analog inputs
 - ▶ Include an amplifier for both headphones and unpowered speakers
 - ▶ Standalone or computer-controlled operation
- 

BASIC FLOW CHART

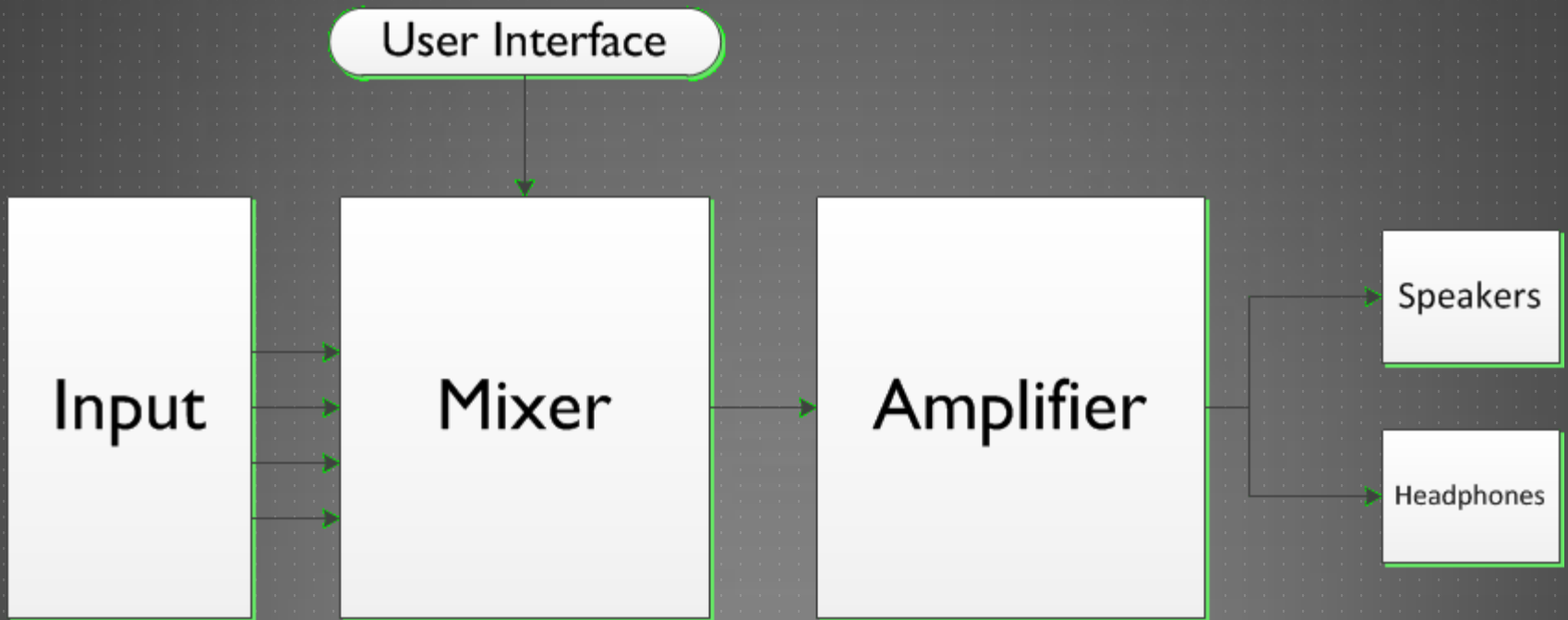

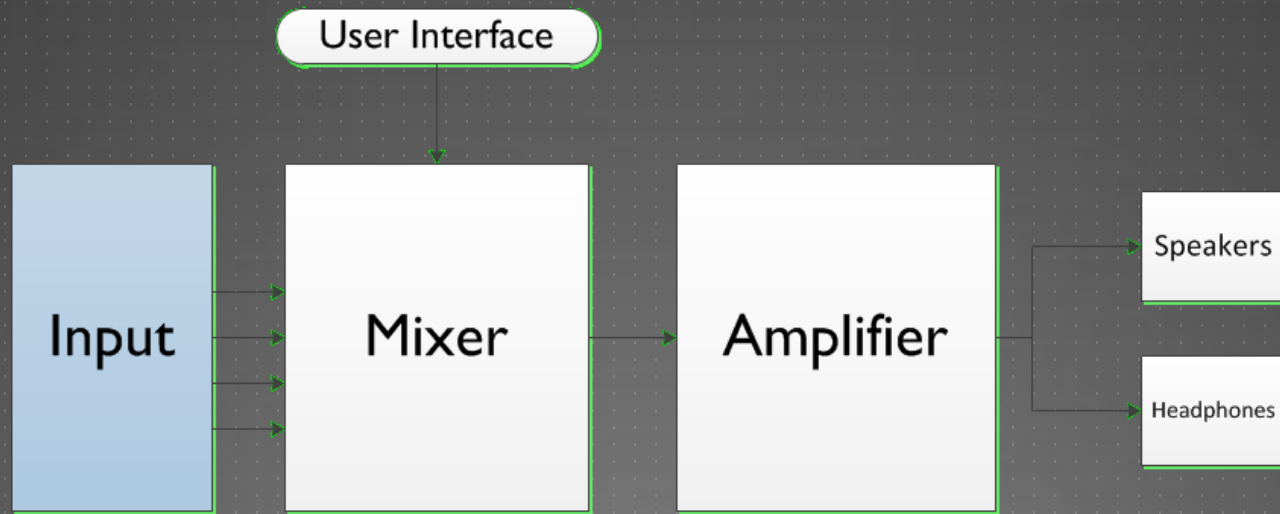

INPUT STAGE

INPUT STAGE

- ▶ Digital to Analog Converter
- ▶ Amplify any signal to 2.5v

DIGITAL TO ANALOG CONVERTER

▶ Main Components

- ▶ IC PCM2902

- ▶ IC LP2951CM


- ▶ 12 MHz Crystal

LP2951CM

► Features

- Low dropout voltage
- Low quiescent current
- High accuracy output voltage
- Easily Available

PIN Configuration

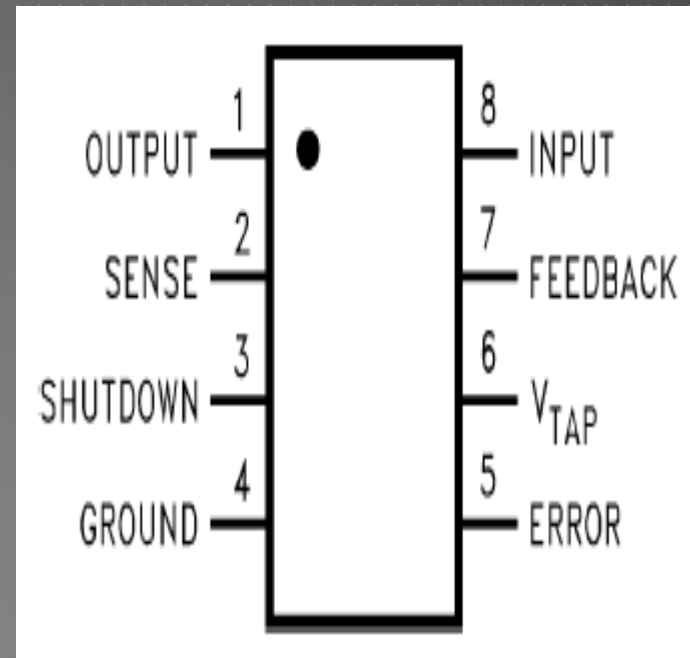

PCM2902


► Features

- Multifunction
- Needs no software
- USB adaptive mode for playback
- Bus powered
- Not depend on operating speed


PIN Configuration

D+	<input type="checkbox"/>	1	28	<input type="checkbox"/>	SSPND
D-	<input type="checkbox"/>	2	27	<input type="checkbox"/>	V _{DDI}
V _{BUS}	<input type="checkbox"/>	3	26	<input type="checkbox"/>	DGND
DGNDU	<input type="checkbox"/>	4	25	<input type="checkbox"/>	DOUT
HID0	<input type="checkbox"/>	5	24	<input type="checkbox"/>	DIN
HID1	<input type="checkbox"/>	6	23	<input type="checkbox"/>	V _{CCXI}
HID2	<input type="checkbox"/>	7	22	<input type="checkbox"/>	AGNDX
SEL0	<input type="checkbox"/>	8	21	<input type="checkbox"/>	XTI
SEL1	<input type="checkbox"/>	9	20	<input type="checkbox"/>	XTO
V _{CCCI}	<input type="checkbox"/>	10	19	<input type="checkbox"/>	V _{CCP2I}
AGNDC	<input type="checkbox"/>	11	18	<input type="checkbox"/>	AGNDP
V _{INL}	<input type="checkbox"/>	12	17	<input type="checkbox"/>	V _{CCP1I}
V _{INR}	<input type="checkbox"/>	13	16	<input type="checkbox"/>	V _{OUTL}
V _{COM}	<input type="checkbox"/>	14	15	<input type="checkbox"/>	V _{OUTR}


DIGITAL TO ANALOG CONVERTER

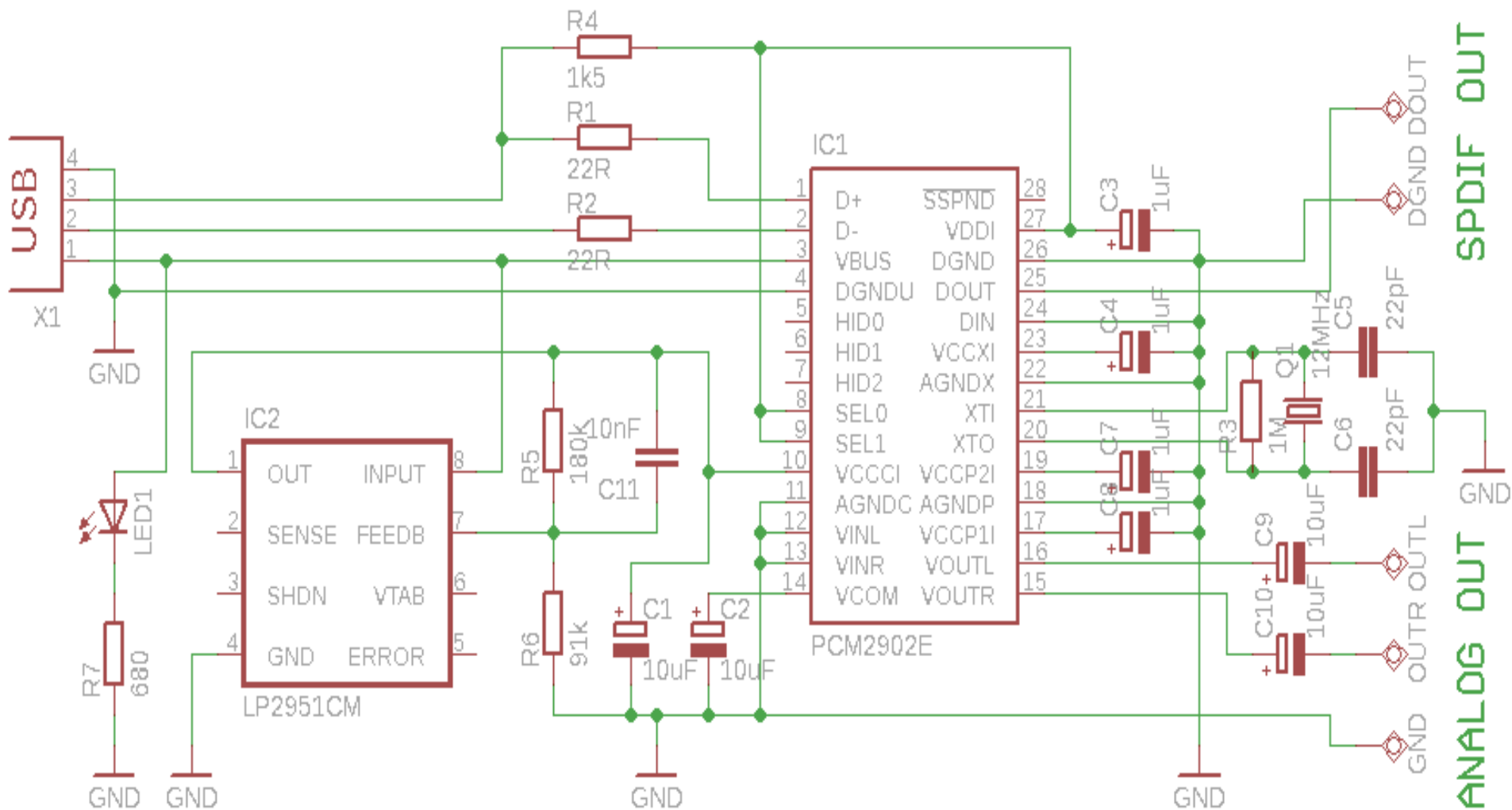


DAC BREAD BOARDED CIRCUIT

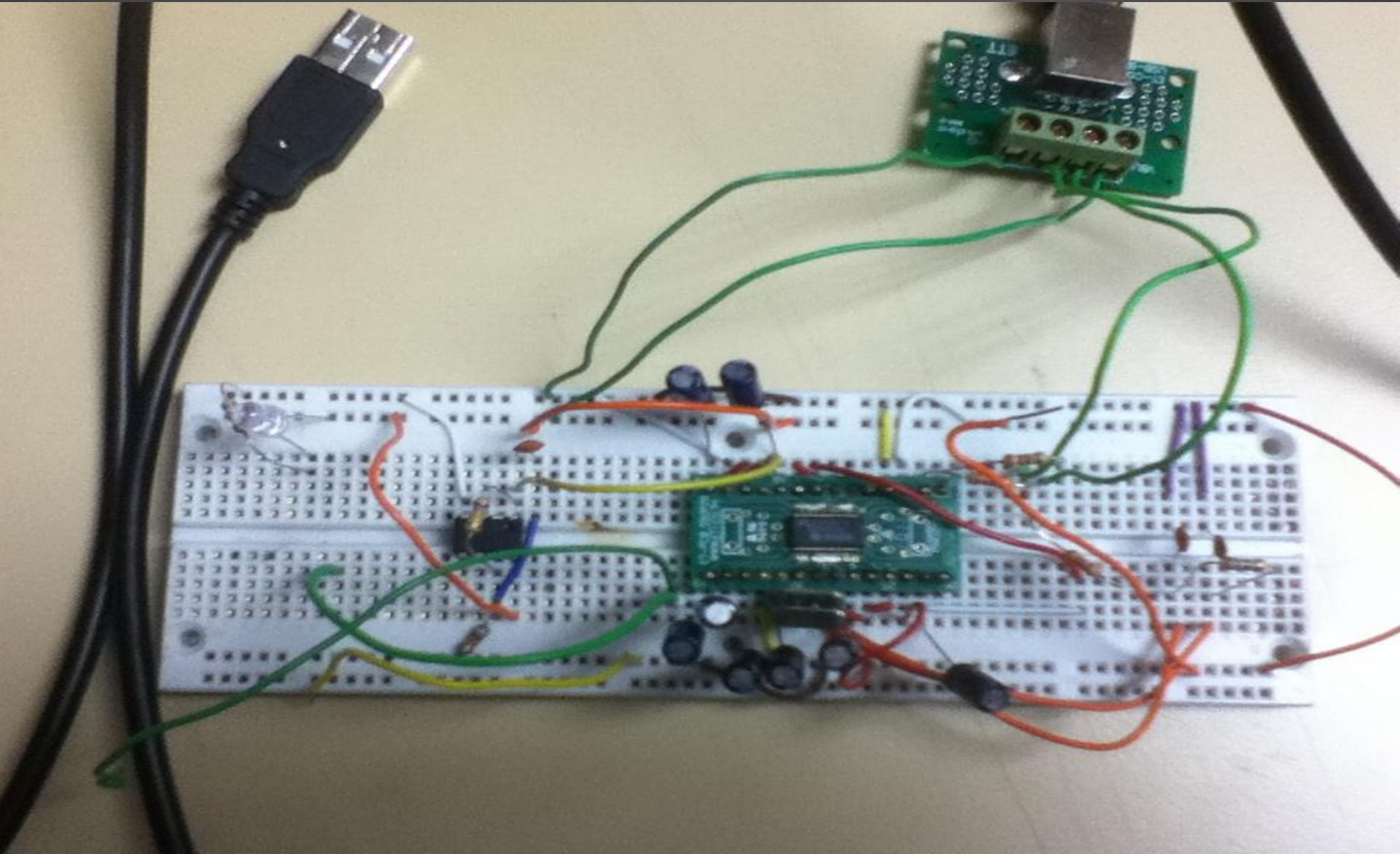

2.5V OUTPUT CIRCUIT

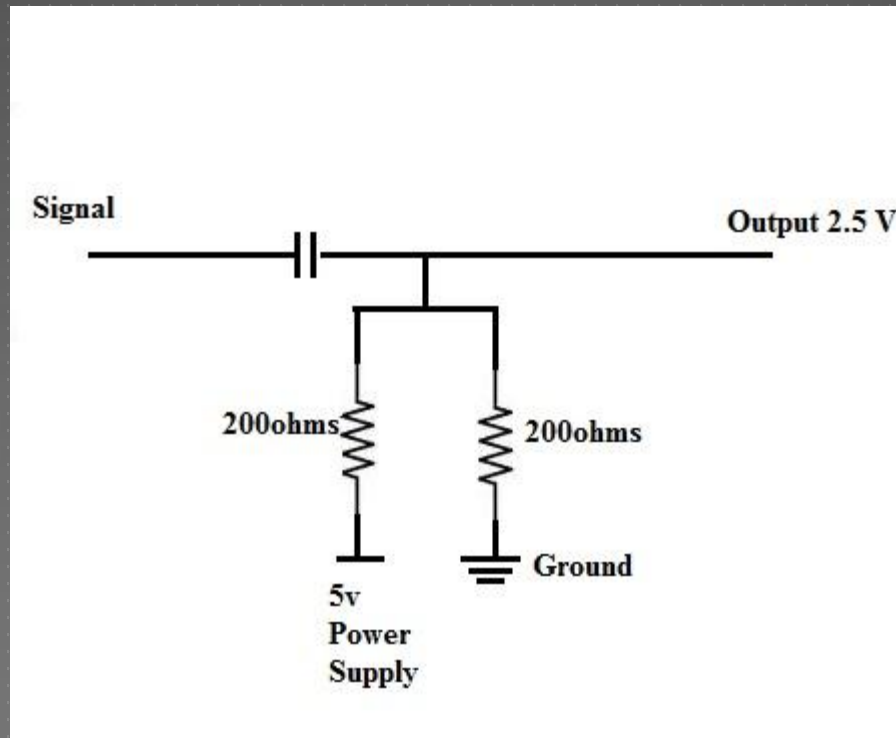

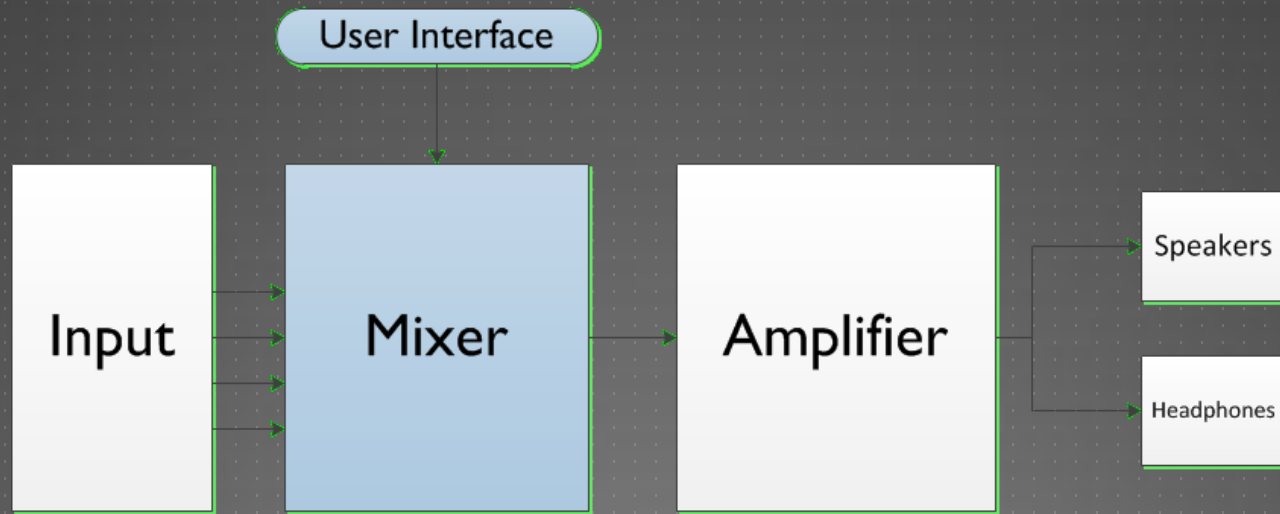

MIXER STAGE

MAIN COMPONENTS

- ▶ Digital potentiometers
 - ▶ Dallas Semi. DS1807
 - ▶ Use I2C to communicate
- ▶ Arduino Duemilanove
 - ▶ Based on an Atmel 328 chip (similar to PIC)
 - ▶ Existing “Wire” library for I2C communication
 - ▶ Simplified USB-based prototyping board

ARDUINO


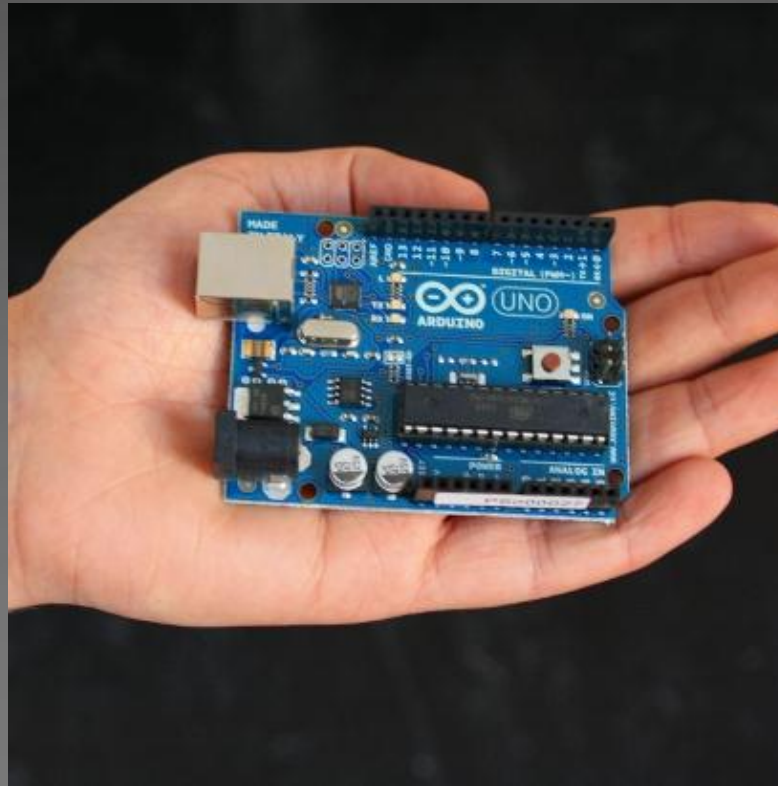


Image provided by www.arduino.cc

ARDUINO

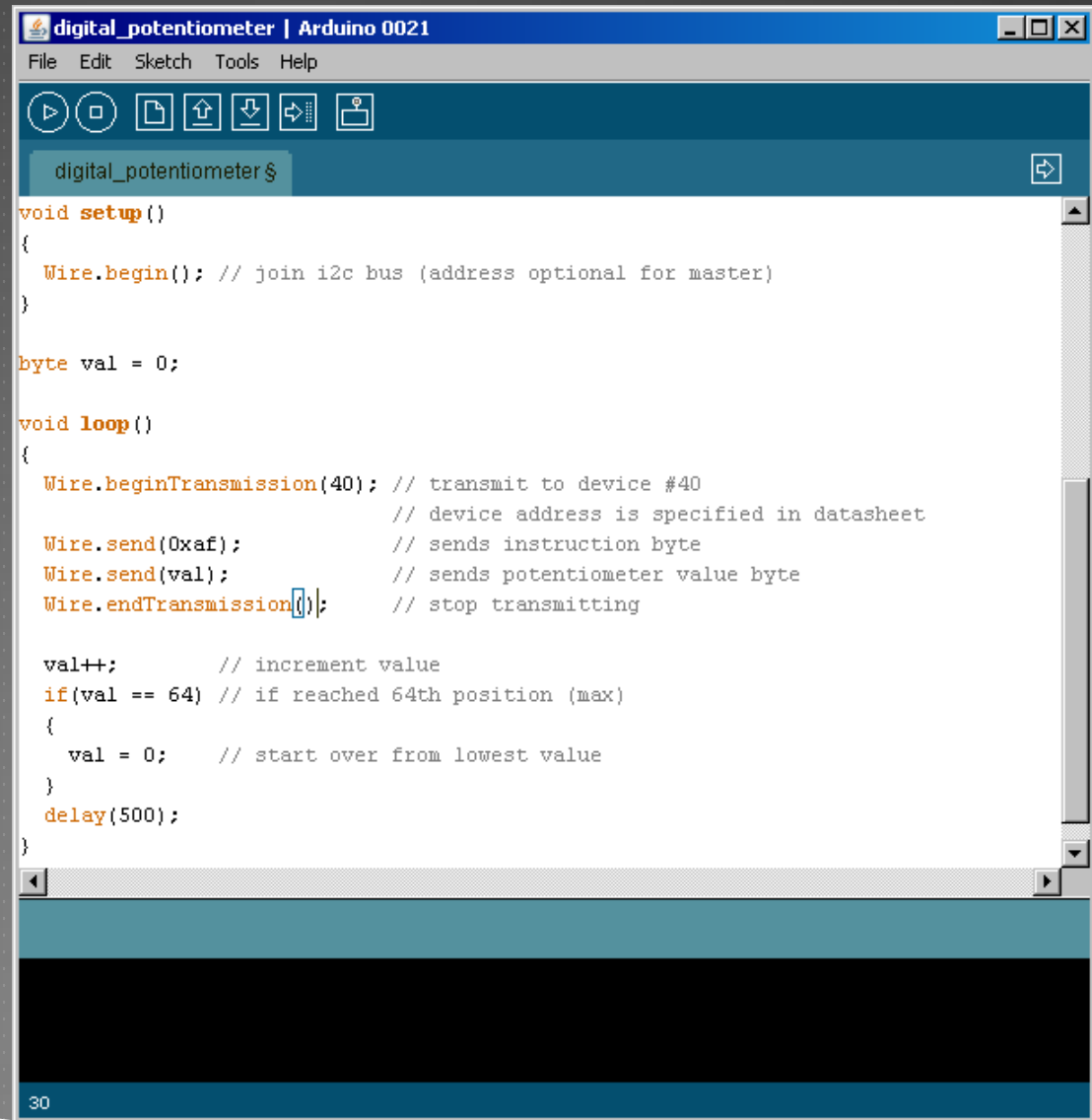- ▶ Freely available IDE and compiler
- ▶ Very easy to use programming language (C++-like)
- ▶ Example program shown with Wire library for I²C communication



The screenshot shows the Arduino IDE interface with a file named "digital_potentiometer | Arduino 0021". The code is written in C++ and uses the Wire library for I2C communication. The code is as follows:

```
void setup()
{
  Wire.begin(); // join i2c bus (address optional for master)
}

byte val = 0;

void loop()
{
  Wire.beginTransmission(40); // transmit to device #40
                               // device address is specified in datasheet
  Wire.send(0xaf);             // sends instruction byte
  Wire.send(val);              // sends potentiometer value byte
  Wire.endTransmission();      // stop transmitting

  val++;                       // increment value
  if(val == 64) // if reached 64th position (max)
  {
    val = 0; // start over from lowest value
  }
  delay(500);
}
```

The IDE interface includes a menu bar (File, Edit, Sketch, Tools, Help), a toolbar with icons for running, stopping, saving, and uploading, and a status bar at the bottom showing the line number 30.

I²C DIGITAL POTENTIOMETERS

► Advantages of I²C Bus

- Bus architecture allows for one set of communication lines
- Components only respond if they are told to (compared to SPI)
- Each device is individually addressable


► Disadvantages

- Protocol overhead – you can't write to all the chips at once, you have to go one at a time
- Requires more processing to write an instruction (speed/latency)

I²C DIGITAL POTENTIOMETERS

- ▶ Chip: Dallas Semiconductor DS1807

PIN ASSIGNMENT

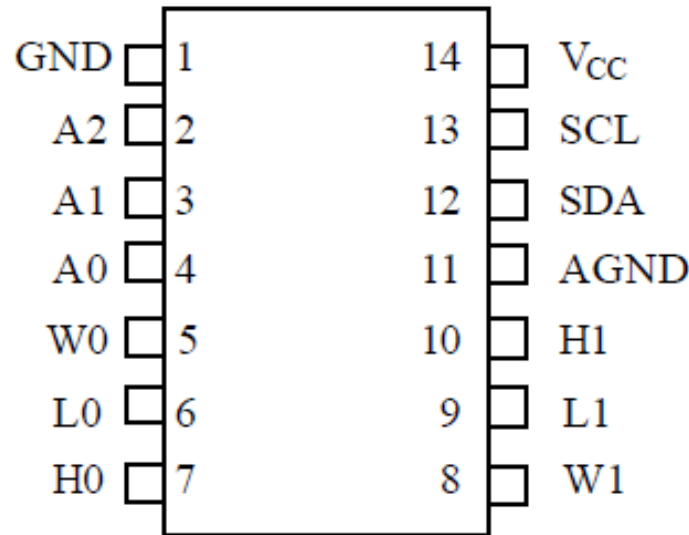


DS1807 14-Pin DIP (300-mil)

I²C DIGITAL POTENTIOMETERS


- ▶ Chip: Dallas Semiconductor DS1807
 - ▶ Designed for audio applications
 - ▶ Log taper – 1 dB increments, 65 total
 - ▶ Readily available from Digi-key


SCHEMATIC

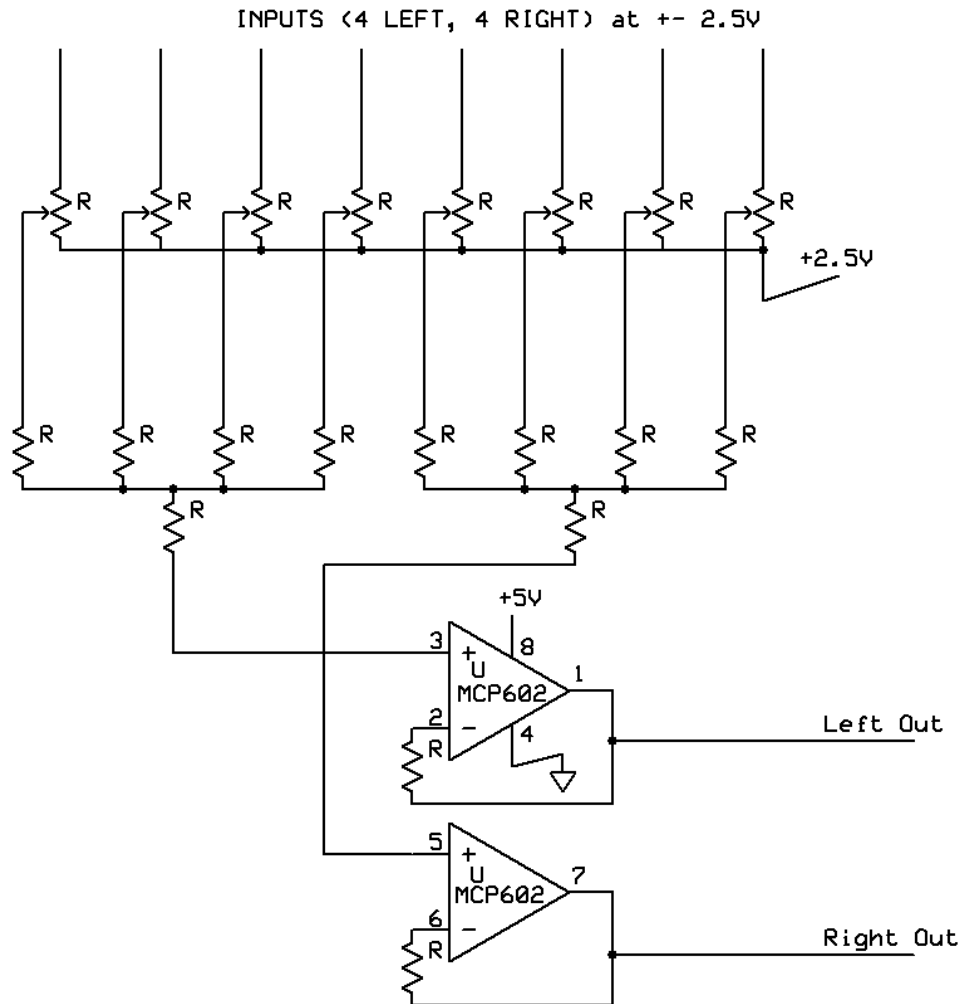

- Inputs are designed to be from the Input Stage
- 2.5V supply provides ground
- MCP602 Op-Amp is set up as a summing amplifier.
- All passive resistors are of 820K value. IM was used in reference design, but 820K was readily available.

PICTURE – INPUT AND MIXER

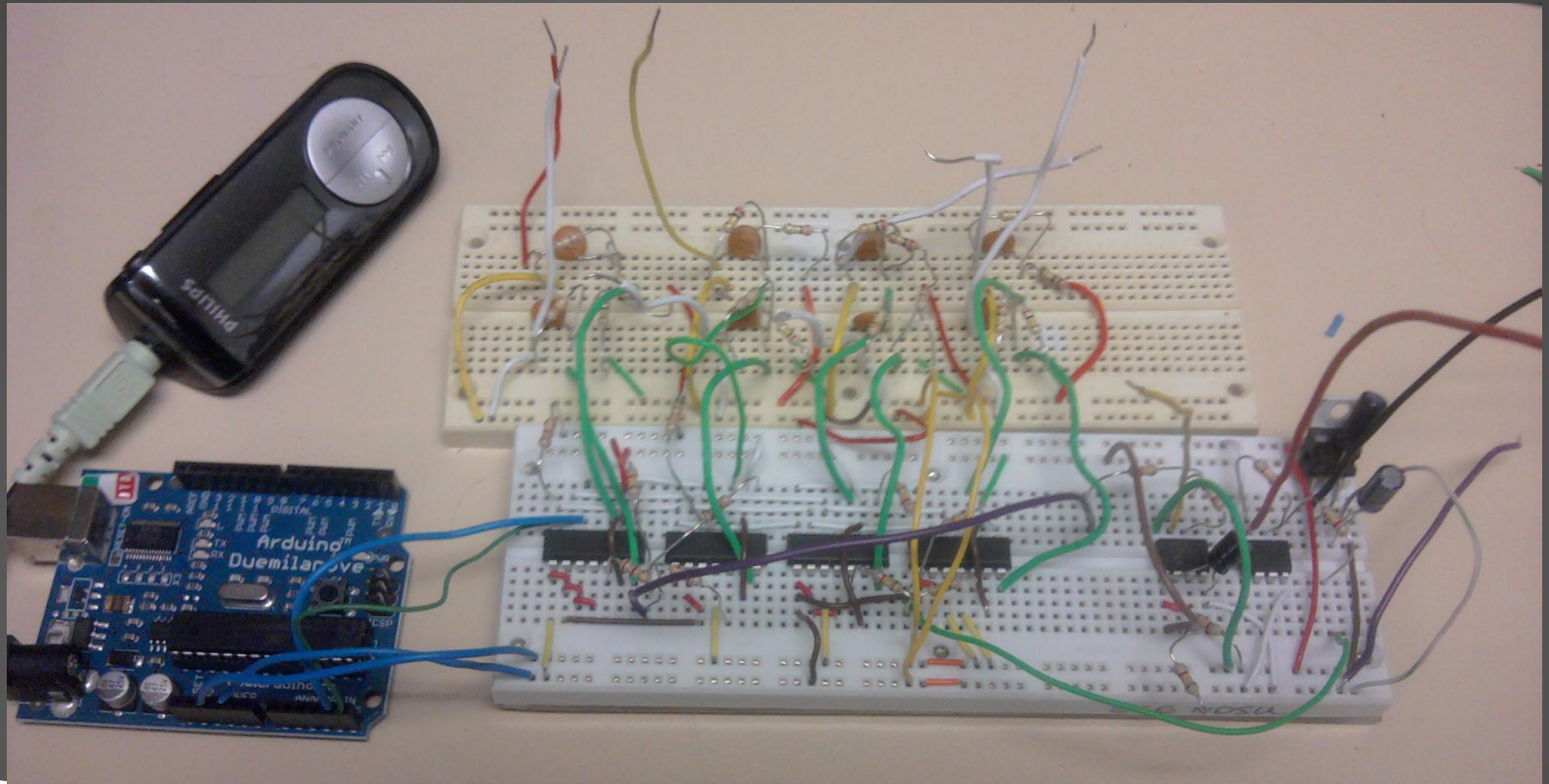

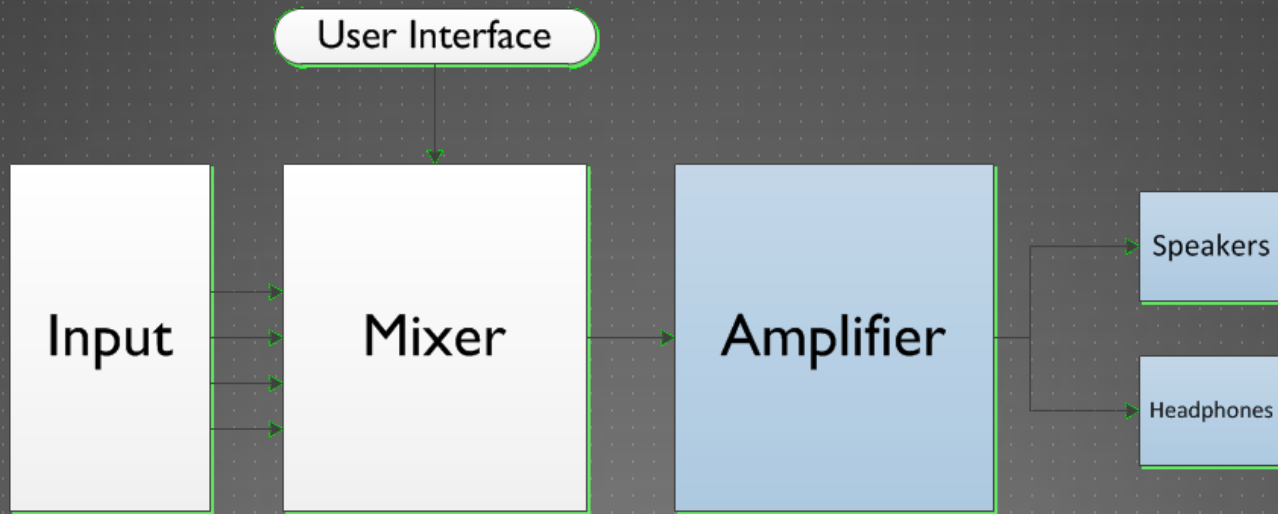

AMPLIFIER STAGE

AMPLIFIER STAGE


- ▶ Headphone Amplifier

- ▶ Uses LM386 for amplifier
- ▶ Design based off of minimum parts design in application section of datasheet


- ▶ Speaker Amplifier

- ▶ Uses STA540 for amplifier
- ▶ Design based off of dual bridge application circuit in datasheet
- ▶ Uses LF353N op-amp for input buffer
- ▶ Design based off of STA540 audio amplifier kit from Sparkfun Electronics

HEADPHONE AMPLIFIER SCHEMATIC

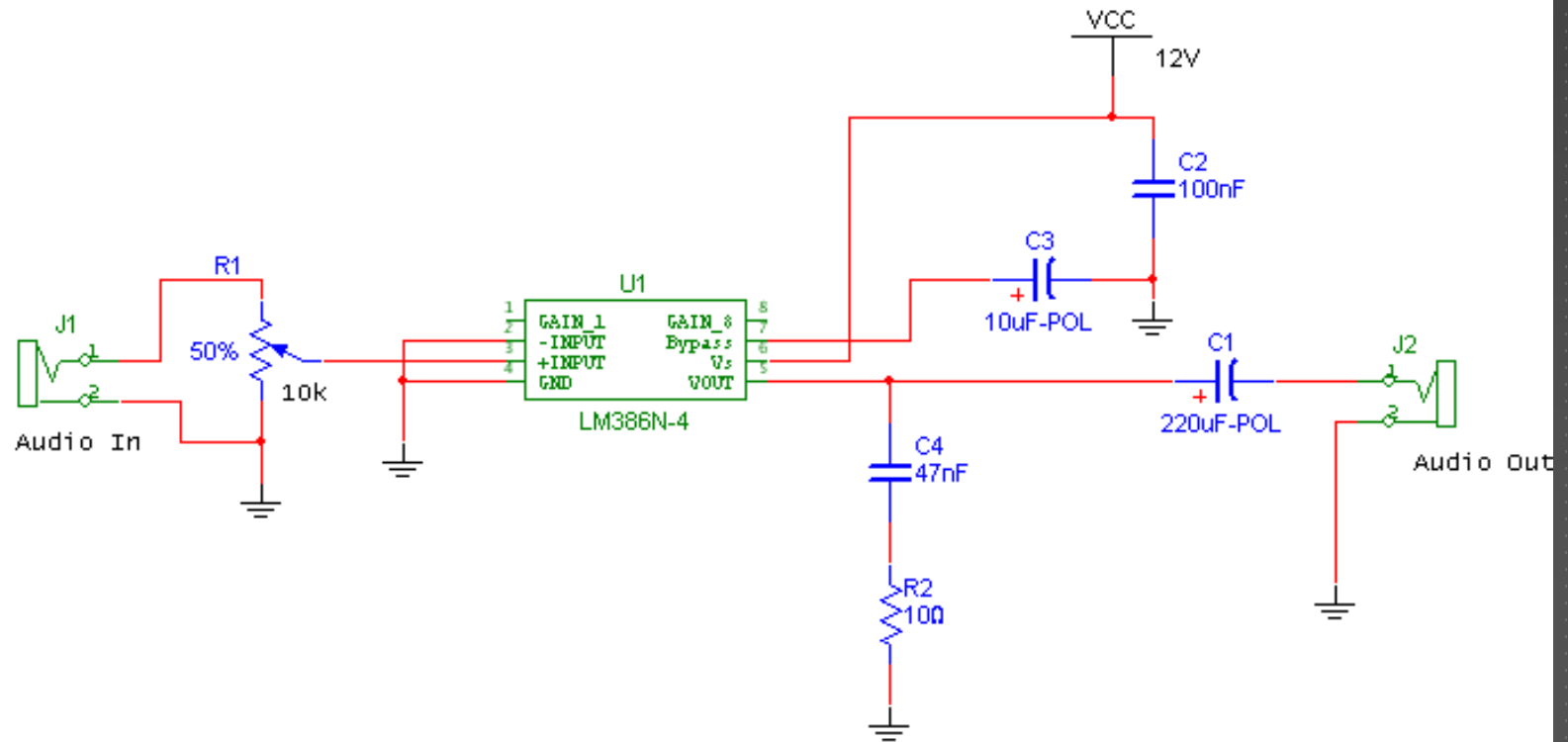

SPEAKER AMPLIFIER SCHEMATIC

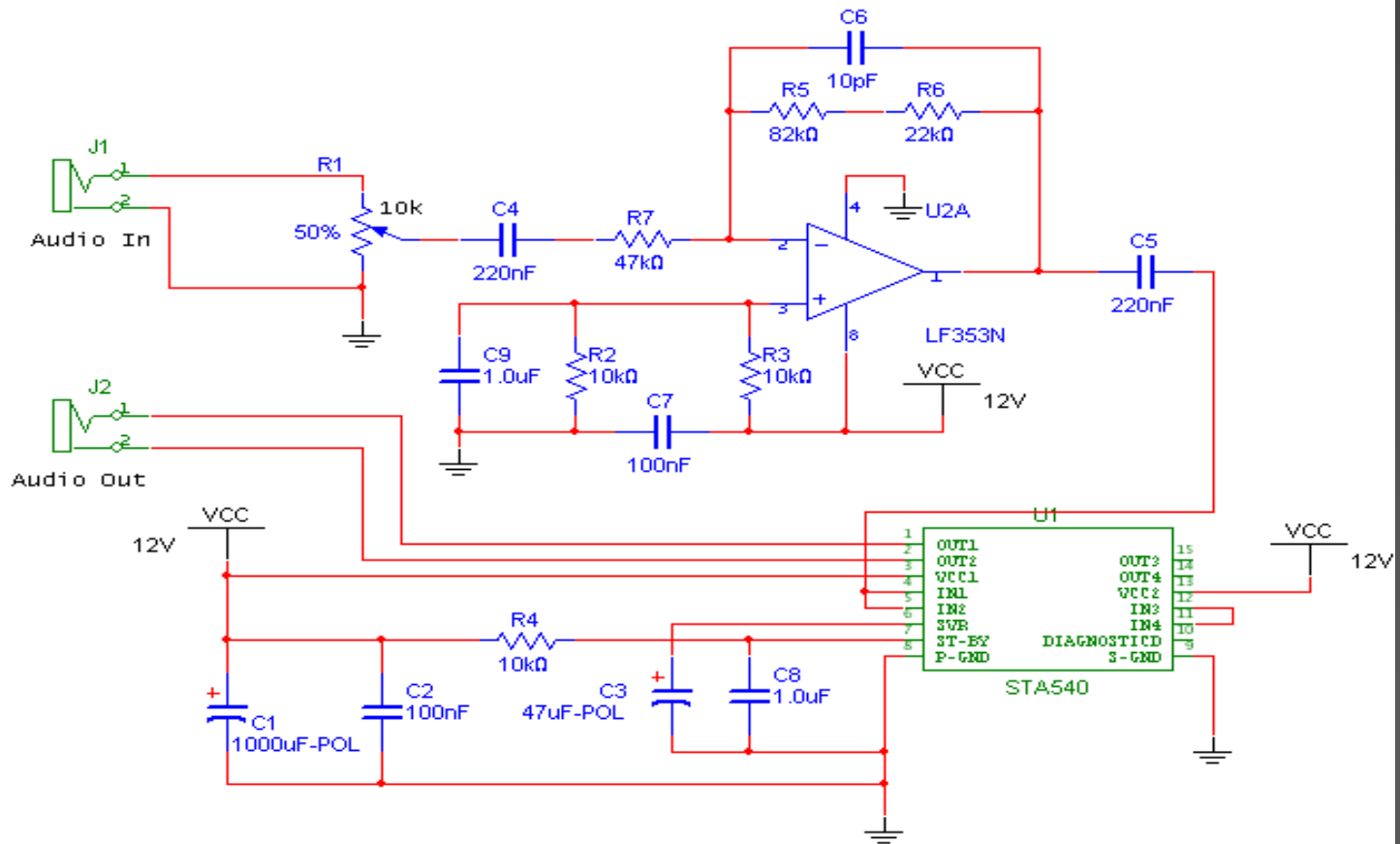

PROJECT STATUS

▶ Input Stage

- ▶ ~~Amplify any signal to 2.5v~~
- ▶ ~~Analog to digital converter~~
- ▶ Duplicated Analog to Digital converter

▶ Mixer Stage

- ▶ ~~Selection of digital potentiometers~~
- ▶ ~~Interface digital potentiometers with Arduino~~
- ▶ ~~Build mixing circuit~~
- ▶ User Interface
 - ▶ LCD
 - ▶ Rotary Encoders

▶ Amplifier Stage

- ▶ ~~Headphone amplifier for single channel~~
- ▶ ~~Speaker amplifier for single channel~~
- ▶ Add headphone amplifier for second channel
- ▶ Modify speaker amplifier to support two channels
- ▶ Add +12V voltage regulators and extensive filtering to reduce noise from power supply
- ▶ Design lowpass filters for audio input to reduce noise from digital electronics in previous stages

BUDGET

Name	Quantity	Unit	Total	Retail
10K digital pot	5	2.4	12	12
10K Audio Pot I2C	5	7.32	36.6	36.6
Rotary Encoder	5	3.6	18	18
PCM2900E SSOP	2	12.34	24.68	24.68
LP2951	2	0.6	1.2	1.2
12MHz Crystal	2	0.4	0.8	0.8
LM386 1W mono amp	2	0.95	1.9	1.9
IC Amp Stereo Headphone	1	2.55	2.55	2.55
STA540 IC Amp	1	3.34	3.34	3.34
LM4766 IC stereo 40W audio amp	1	6.5	6.5	6.5
LM4765 IC stereo 30W audio amp	1	7.45	7.45	7.45
Heatsink	1	1.98	1.98	1.98
10k Ohm linear rotary potentiometer	4	0.96	3.84	3.84
Arduino USB Board	2	30.00	60.00	60.00
Resistors, Capacitors	--	--	0 (In house)	Estimated \$2
Total				182.84

BUDGET

- ▶ Remaining items to purchase:
 - ▶ LCD display (est. \$25)
 - ▶ USB connector (est. \$4)

DESKTOP AUDIO SYSTEM

Questions?